
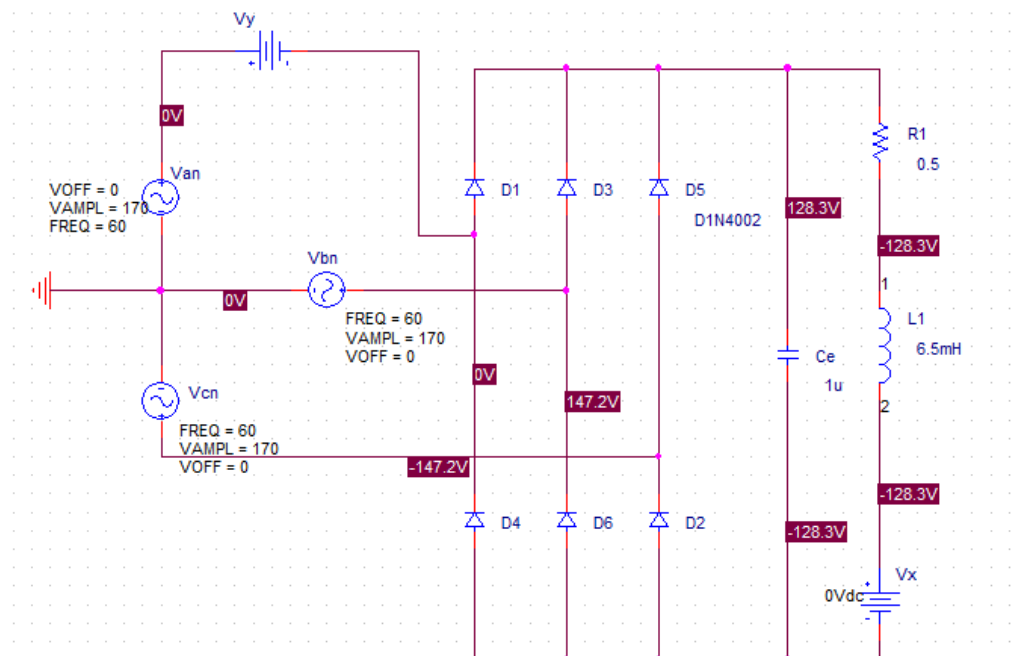


EE-368 Power Electronics

Uncontrolled Three Phase Rectifiers


INTRODUCTION:

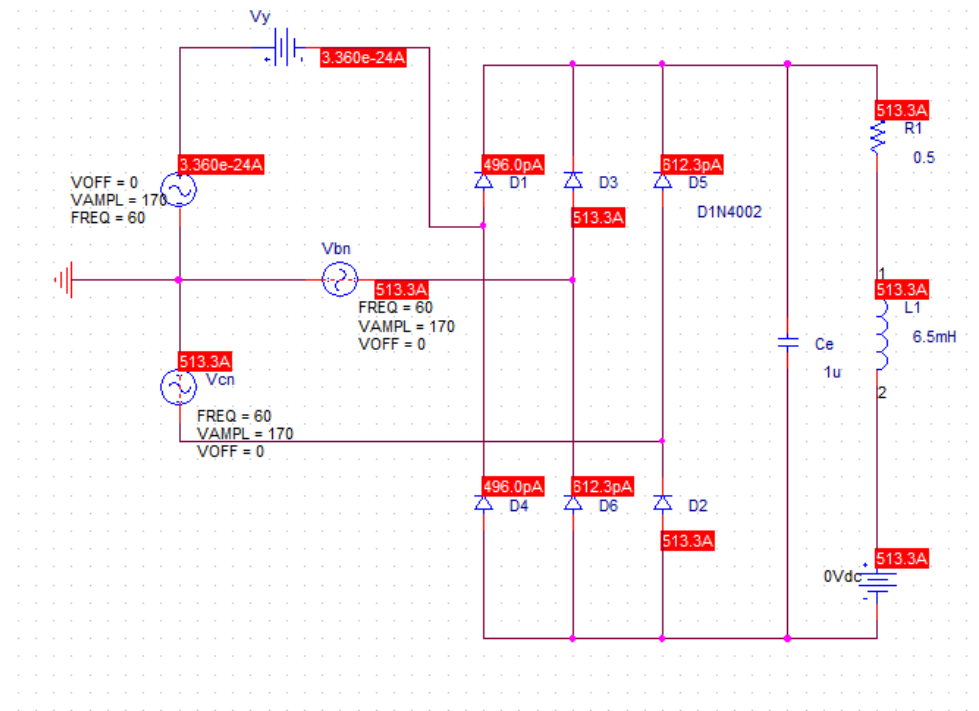In this lab, we will learn about the three phase uncontrolled rectifiers. The circuit of three phase diode rectifier will be implemented in PSPICE. The operation of circuit will be observed alongwith the calculation of different parameters.




Part A


Circuit Diagram PSPICE:

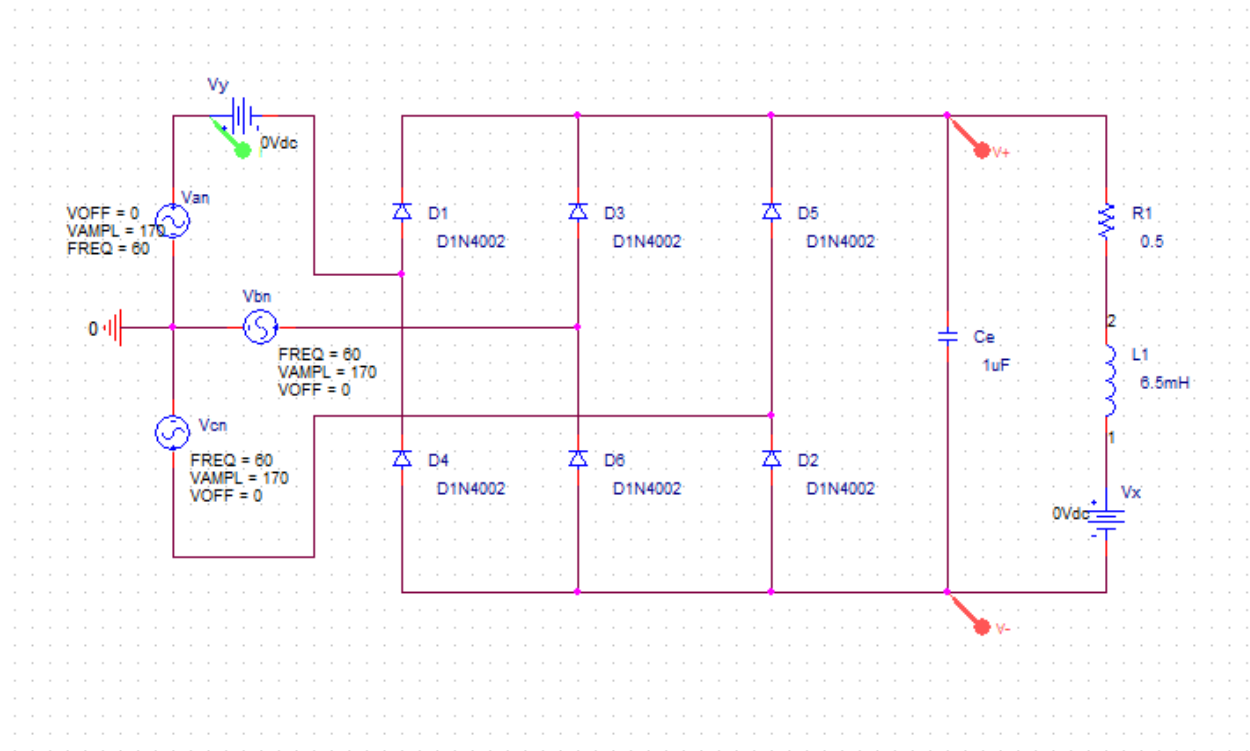


Instantaneous Output voltage

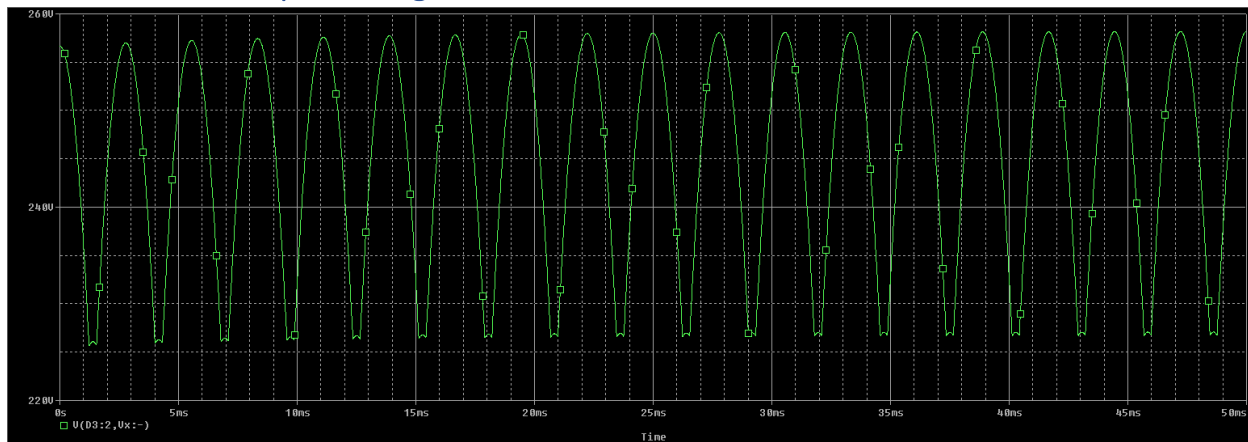

Input line current:

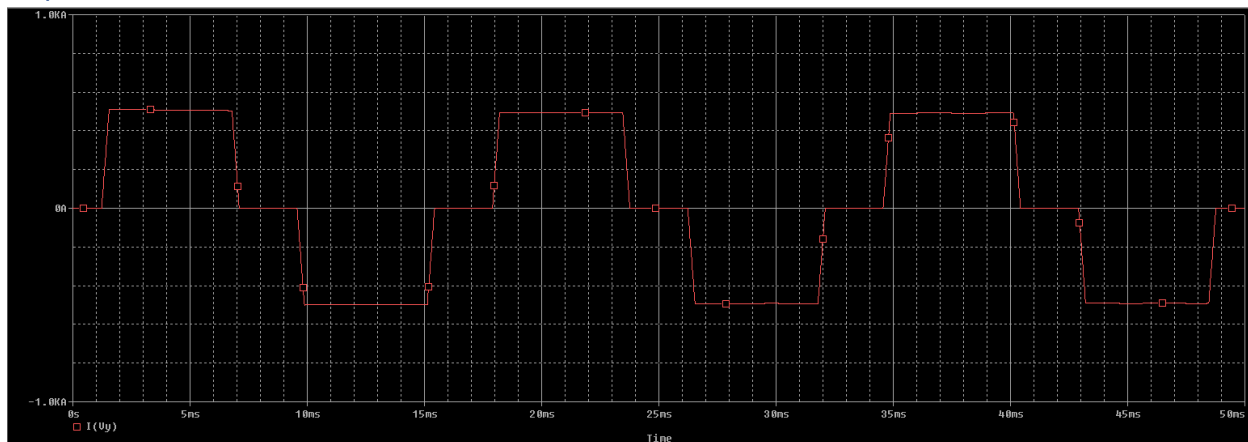


Phase Voltages

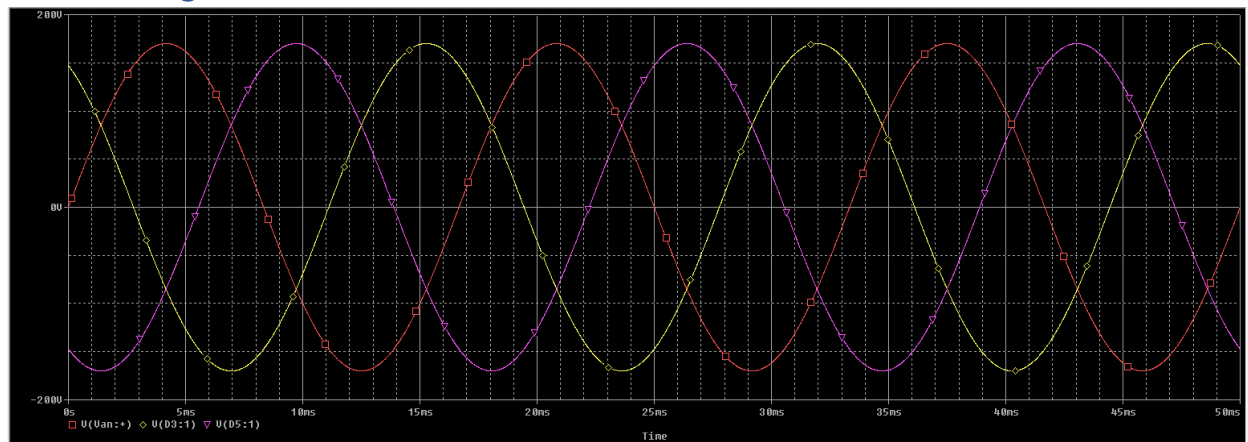


Part B


Circuit Diagram PSPICE:

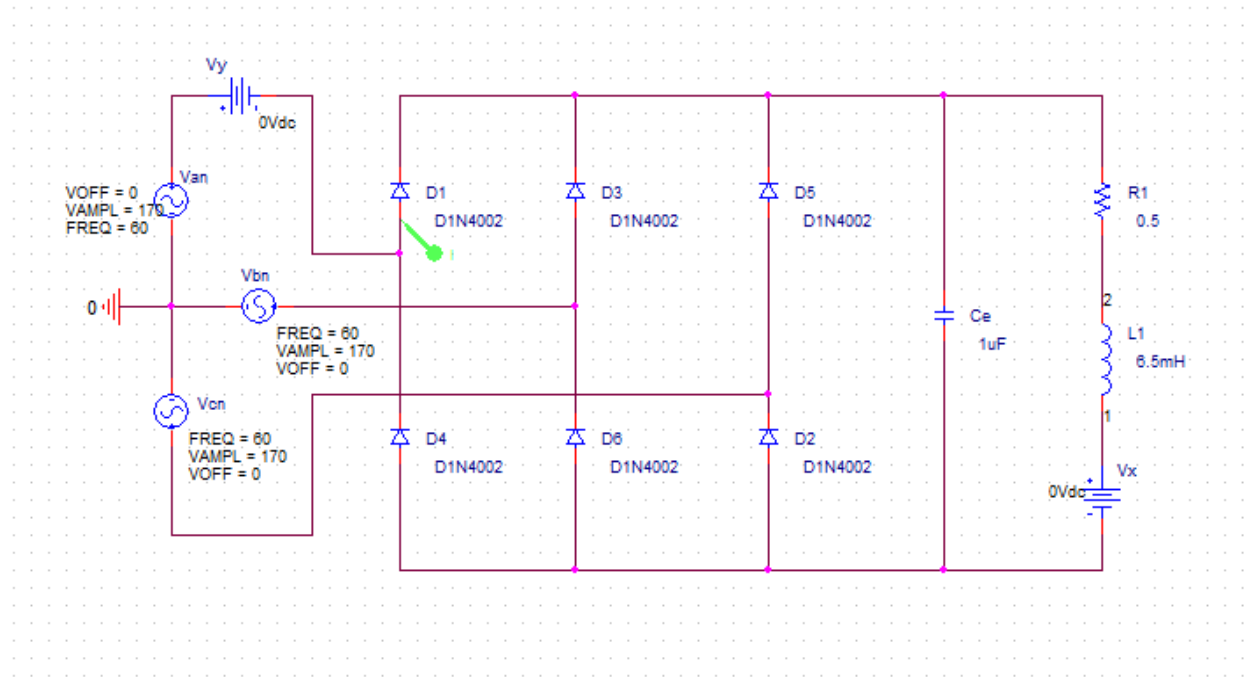

Instantaneous Current Through diode D1

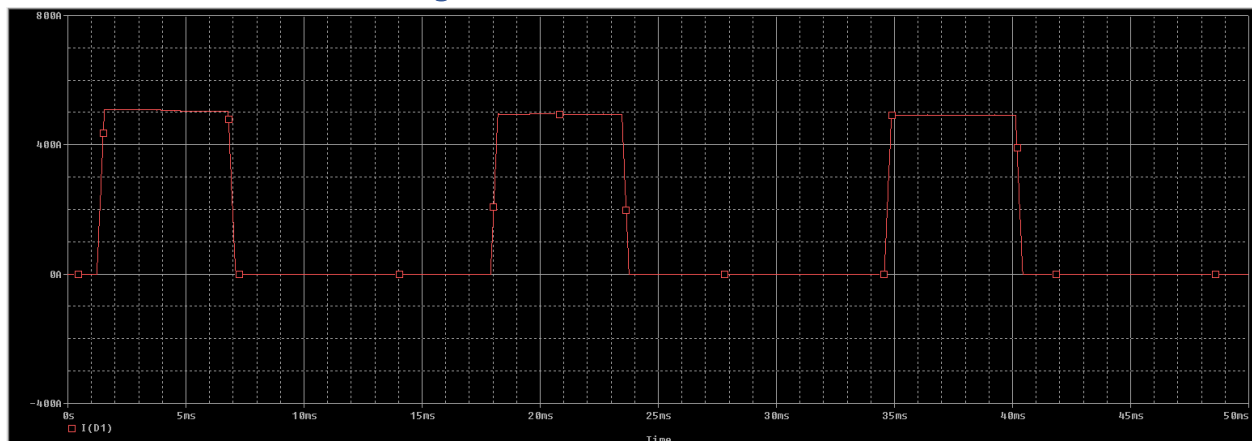


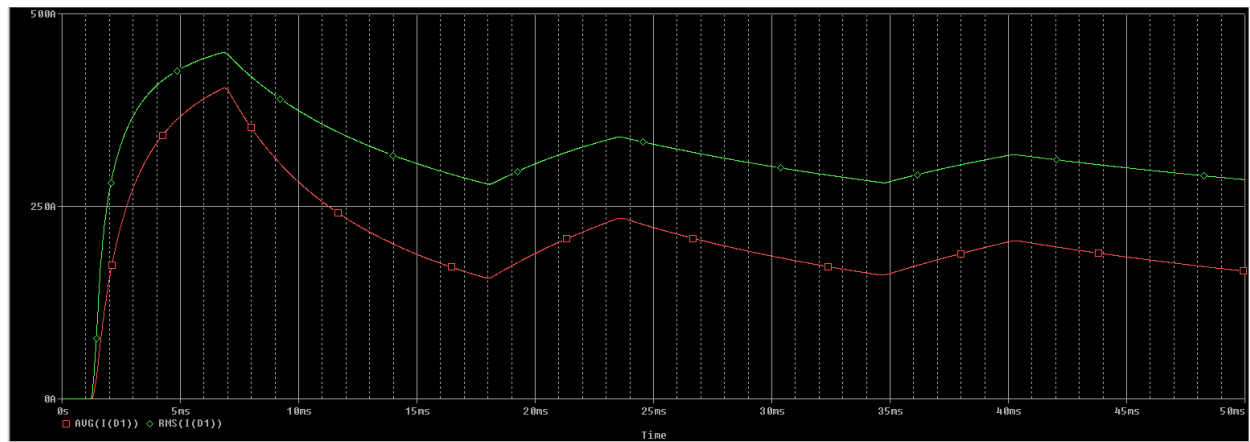Rms and Average Current through diode (D1)




Part C

Circuit Diagram PSPICE:

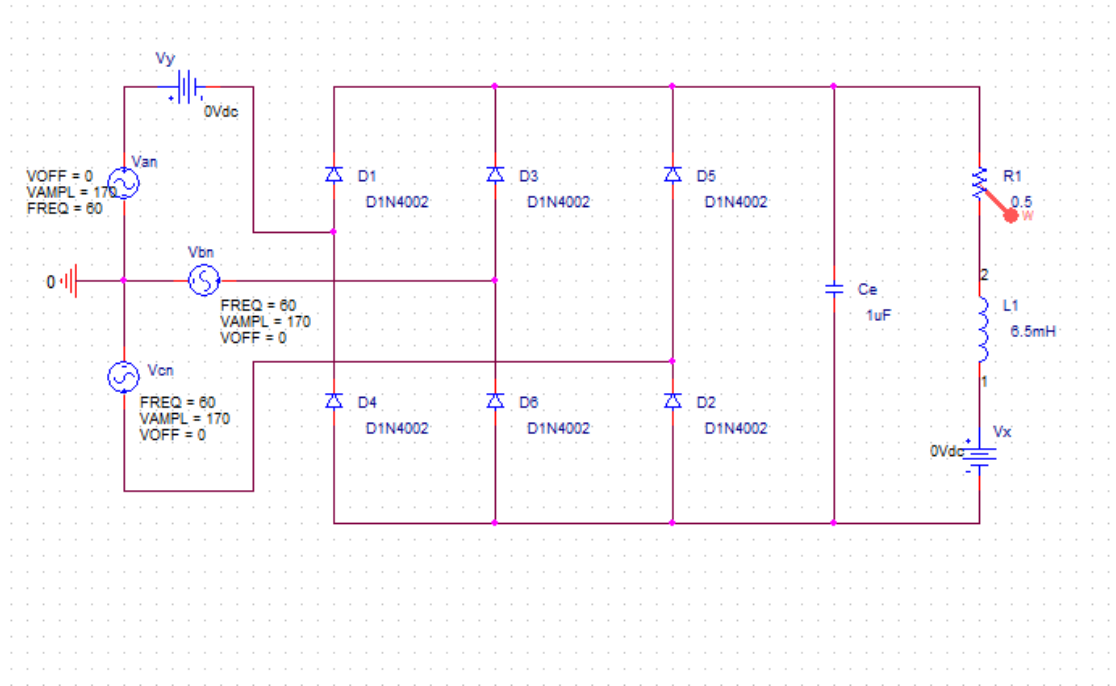

Instantaneous average output power:

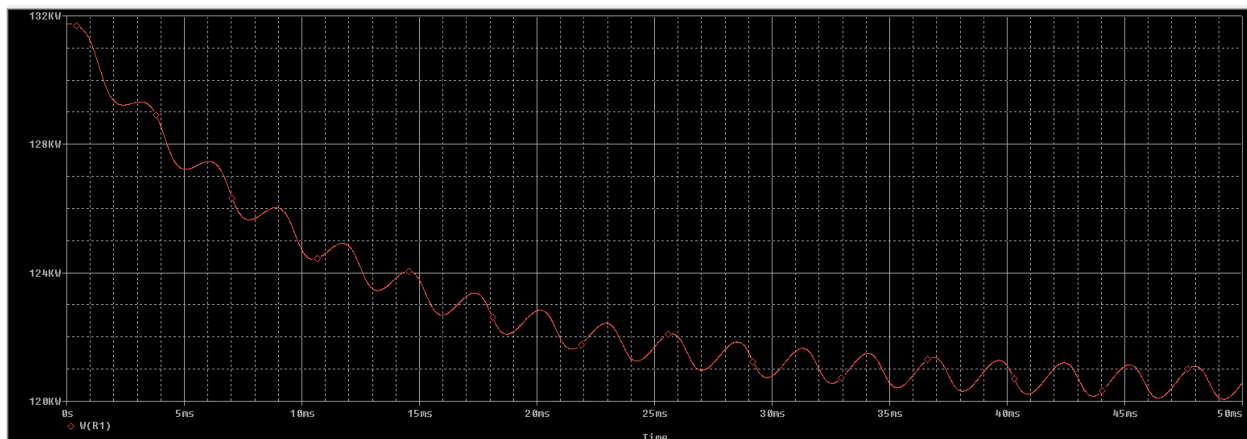

Part D

FFT of the input current:

FOURIER COMPONENTS OF TRANSIENT RESPONSE I(V_Vy)

DC COMPONENT = 1.490506E-01


HARMONIC NO	FREQUENCY (HZ)	FOURIER COMPONENT	NORMALIZED COMPONENT	PHASE (DEG)	NORMALIZED PHASE (DEG)
1	6.000E+01	5.415E+02	1.000E+00	-1.236E-02	0.000E+00
2	1.200E+02	1.255E-01	2.317E-04	-7.605E+01	-7.602E+01
3	1.800E+02	6.606E-02	1.220E-04	-7.946E+01	-7.942E+01
4	2.400E+02	6.138E-02	1.133E-04	-9.510E+01	-9.505E+01
5	3.000E+02	1.069E+02	1.974E-01	1.797E+02	1.798E+02
6	3.600E+02	1.025E-02	1.892E-05	1.796E+02	1.797E+02
7	4.200E+02	7.534E+01	1.391E-01	-1.796E+02	-1.795E+02
8	4.800E+02	2.849E-02	5.260E-05	9.715E+01	9.724E+01
9	5.400E+02	2.082E-02	3.845E-05	1.089E+02	1.090E+02

TOTAL HARMONIC DISTORTION = 2.415301E+01 PERCENT

JOB CONCLUDED

TOTAL JOB TIME .28

□

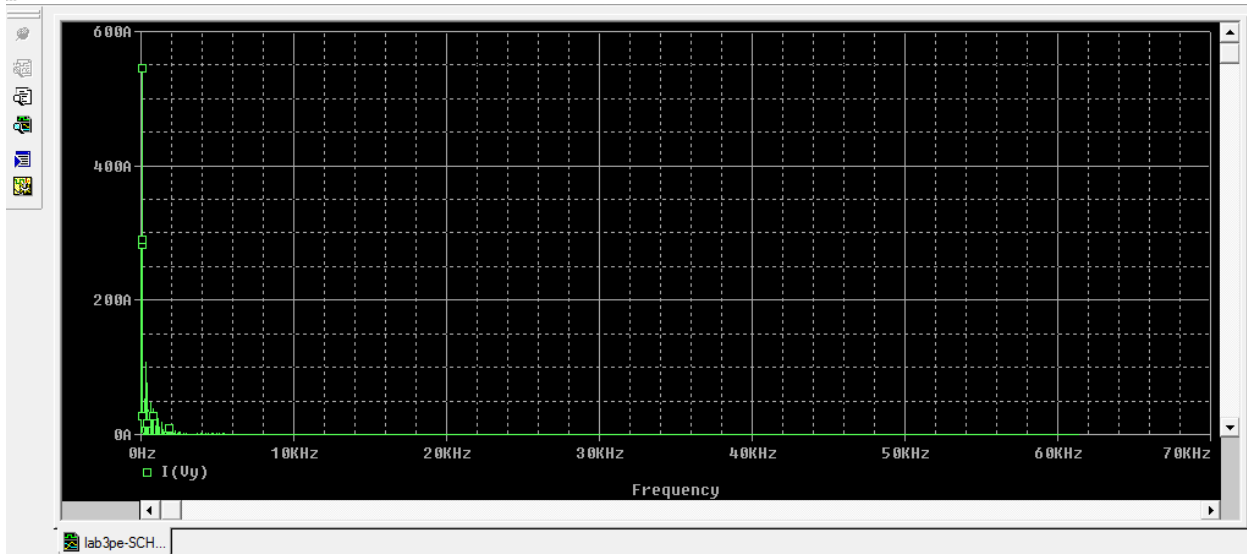

CALCULATIONS:

$I_{IN(DC)} = 1.49E-1$	$I_{1(RMS)} = 3.813E2$
THD (I_{IN}) = 24.15 %	$I_{h(RMS)} = 0.887E2$
$\phi_1 = 0^\circ$.	DF = 1
PF =0.97	

CONCLUSION:

In this lab, we learnt about the three phase uncontrolled rectifiers. The circuit of three phase diode rectifier was implemented in PSPICE. The operation of circuit was observed alongwith the calculation of different parameters.